

UNIT 7

**SEQUENTIAL LOGIC
COUNTERS AND REGISTERS
1ST SESSION**


Registers

- Combination of Flip-flops (FF).
- FF stores 0 or 1, to store multiple bits, multiple FFs-**Register**.
- n FFs are connected in series in order to store n bits of data.
- Information stored within registers can be transferred using **shift registers**.
- **Clock pulse** are used to shift left or right.
- n-bit shift register- made by connecting n FFs.
- Left shift of data- **shift left registers**.
- Right shift of data- **shift right registers**.



Shift register

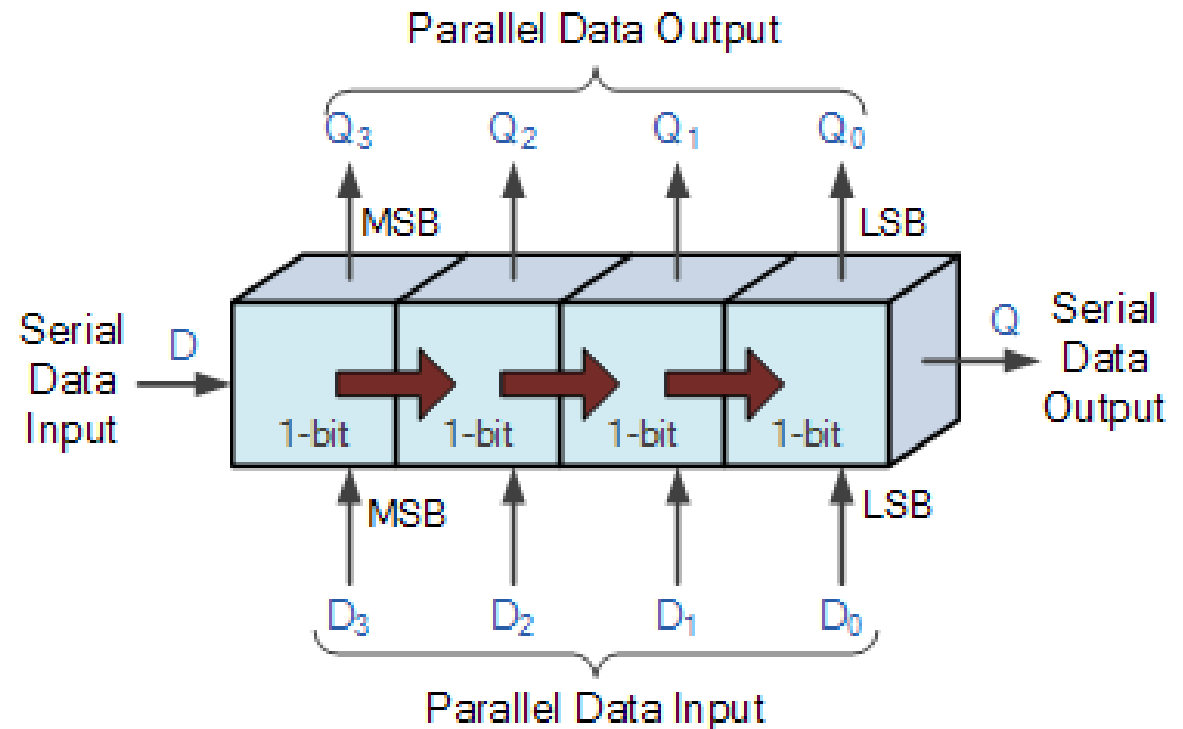- Used for the storage or the transfer of binary data.
- Loads the data present on its inputs and then moves or “shifts” it to its output once every clock cycle, hence the name **Shift Register**.
- Basically consists of several single bit “D-Type Data Latches”.
- Provided with a *clear* or *reset* connection so that they can be ‘*SET*’ or ‘*RESET*’ as required.



Type of shift registers

- i. Serial-in to Parallel-out (SIPO)* - the register is loaded with serial data, one bit at a time, with the stored data being available at the output in parallel form.
- ii. Serial-in to Serial-out (SISO)* - the data is shifted serially “IN” and “OUT” of the register, one bit at a time in either a left or right direction under clock control.
- iii. Parallel-in to Serial-out (PISO)* - the parallel data is loaded into the register simultaneously and is shifted out of the register serially one bit at a time under clock control.
- iv. Parallel-in to Parallel-out (PIPO)* - the parallel data is loaded simultaneously into the register, and transferred together to their respective outputs by the same clock pulse.

Data Movement Through A Shift Register

Clock Pulse No	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0




Fig: Timing Diagram

Operation:

- Lets assume that all the flip-flops (FFA to FFD) have just been RESET (CLEAR input) and that all the outputs Q_A to Q_D are at logic level “0” ie, no parallel data output.
 - i. When ***DATA input=1***, the output of FFA i.e., Q_A is set HIGH (logic “1”) on the ***first clock pulse*** and all the other outputs of remaining FFs will be LOW (logic “0”).
 - ii. The ***second clock pulse*** will change the output of FFA to logic “0” and the output of FFB i.e., Q_B is set HIGH as its input D has the logic “1” level on it from Q_A . *The logic “1” has now moved or been “shifted” one place along the register to the right as it is now at Q_A .*
 - iii. When the ***third clock pulse*** arrives this logic “1” value moves to the output of FFC (Q_C) and so on until the arrival of the ***fifth clock pulse*** which sets all the outputs Q_A to Q_D back again to logic level “0” because the input to FFA has remained constant at logic level “0”.

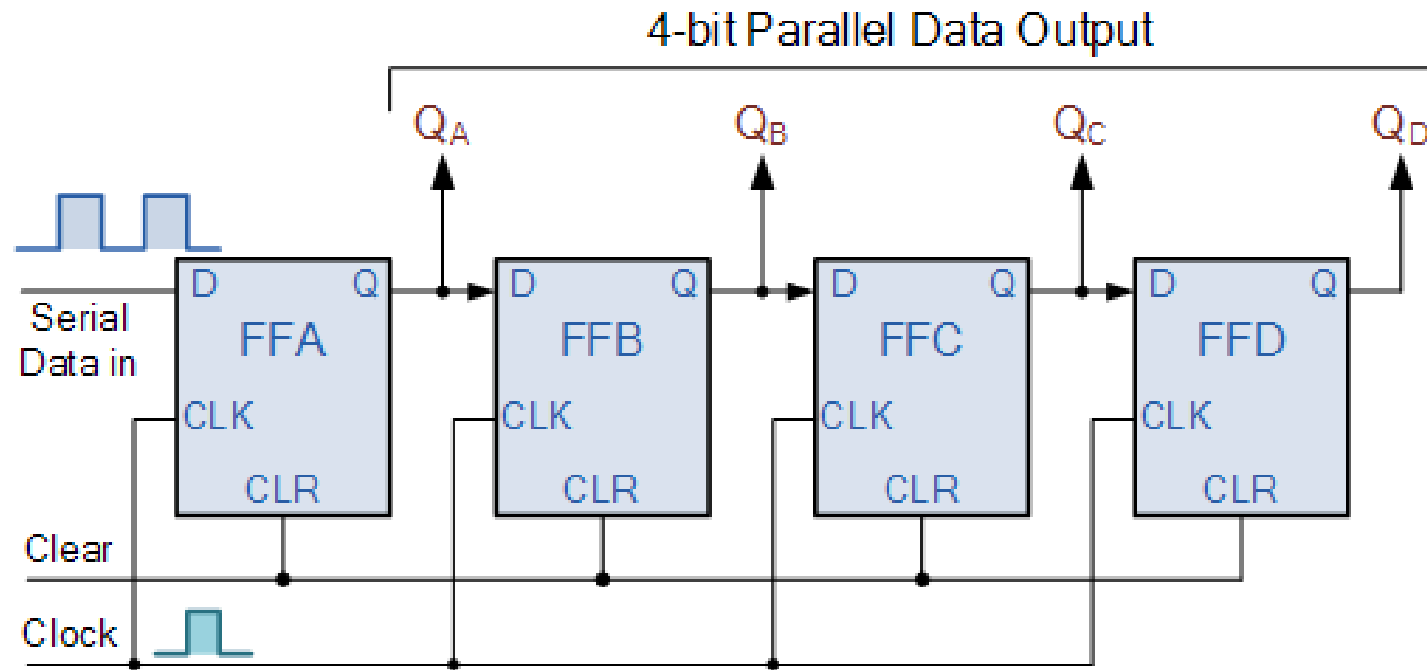i. Serial-in to Parallel-out (SIPO) Shift Register

- **4-bit Serial-in to Parallel-out Shift Register:**



Let the **input data=1101** is to be stored in register. The registers are cleared (0000) initially.

CLK	Register content				Comments
	Q _A	Q _B	Q _C	Q _D	
Initially	0	0	0	0	<i>The LSB enters first.</i> Data is completely stored after the 4 th clock. Output is available all at a time simultaneously.
1 →	1	0	0	0	
2 →	0	1	0	0	
3 →	1	0	1	0	
4 →	1	1	0	1	


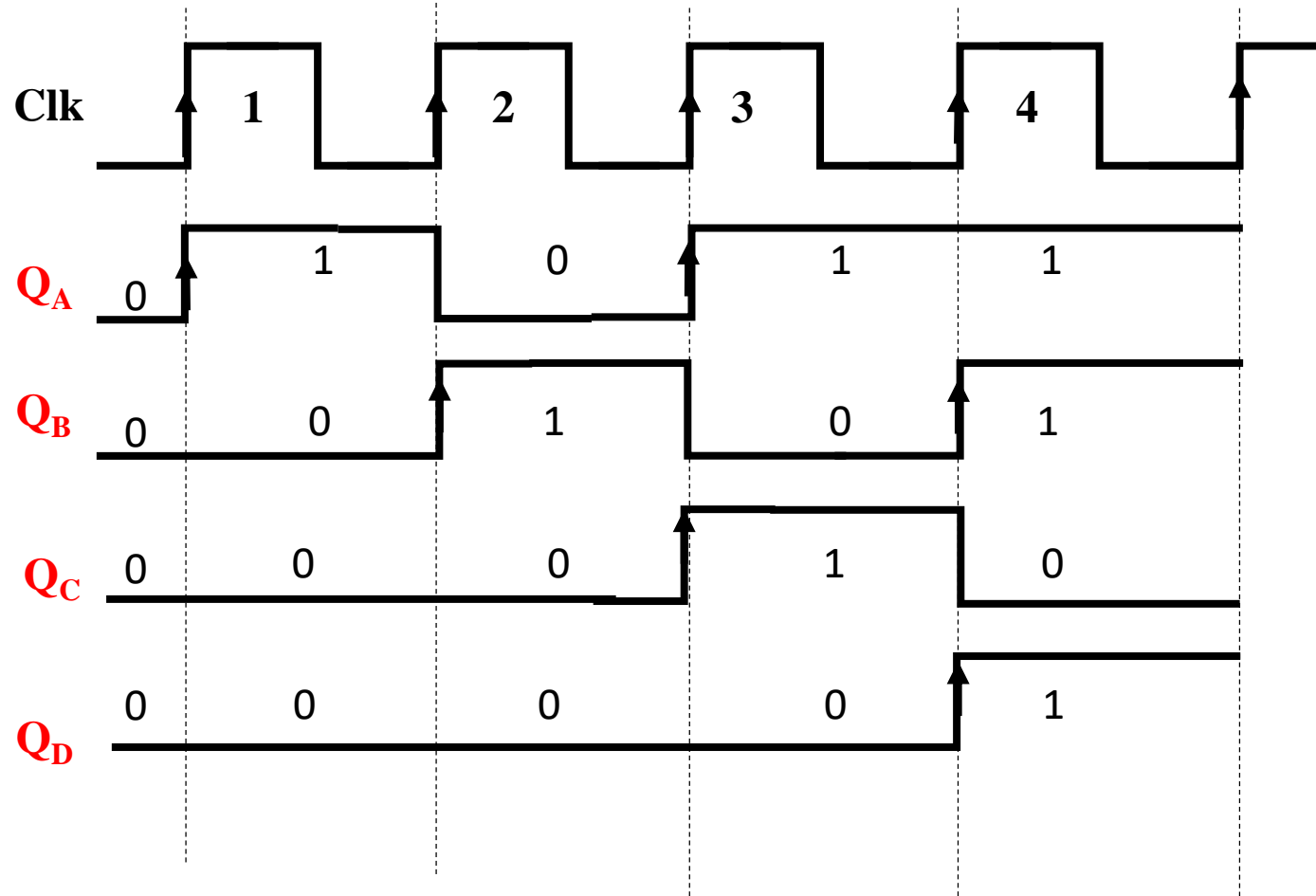


Fig: Timing Diagram for storing 1101 in SIPO shift register

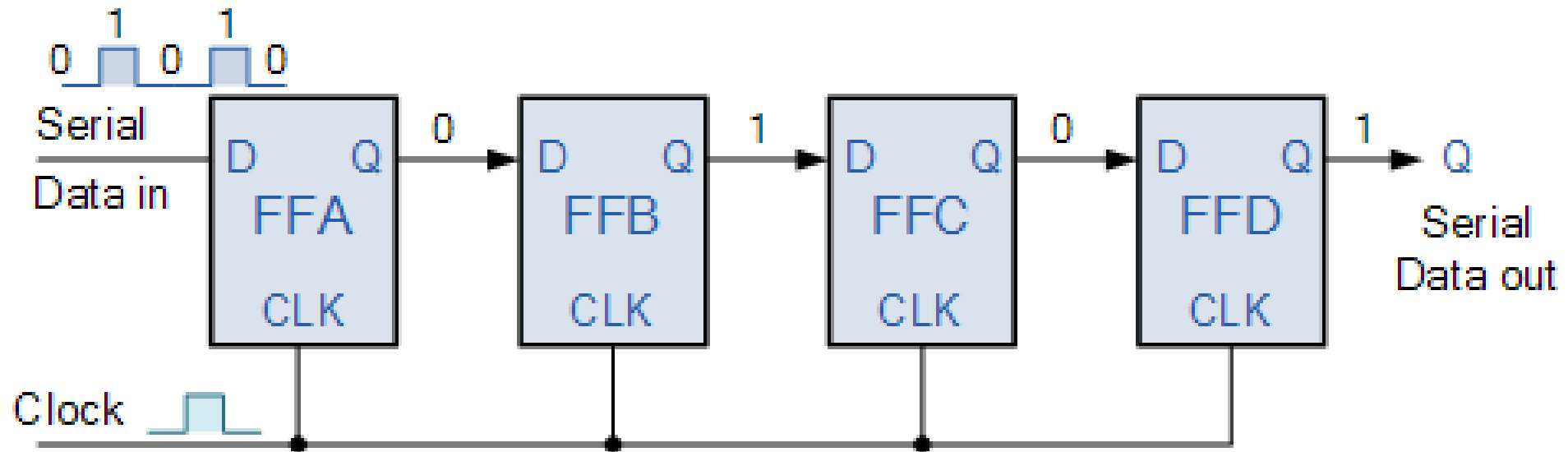ii. *Serial-in to Serial-out (SISO) Shift Register*

- **4-bit Serial-in to Serial-out Shift Register**



- Data is allowed to flow straight through the register and out of the other end.
- Since there is only one output, the DATA leaves the shift register one bit at a time in a serial pattern, hence the name **Serial-in to Serial-Out Shift Register** or **SISO**.

Let's explain the operation of *SISO* by storing and retrieving data-'*1011*'. Initially, let us assume register content is cleared.

Clock	Register Content				Remarks
	Q ₀	Q ₁	Q ₂	Q ₃	
Initially	0	0	0	0	LSB enters first.
1 →	1	0	0	0	
2 →	1	1	0	0	
3 →	0	1	1	0	
4 →	1	0	1	1	All data bits are stored after 4 th clock pulse.
5	0	1	0	1	
6	0	0	1	0	
7	0	0	0	1	Register get cleared after 8 th clock pulse
8	0	0	0	0	


 


Fig: Timing Diagram for storing and retrieving 1011 in SISO shift register

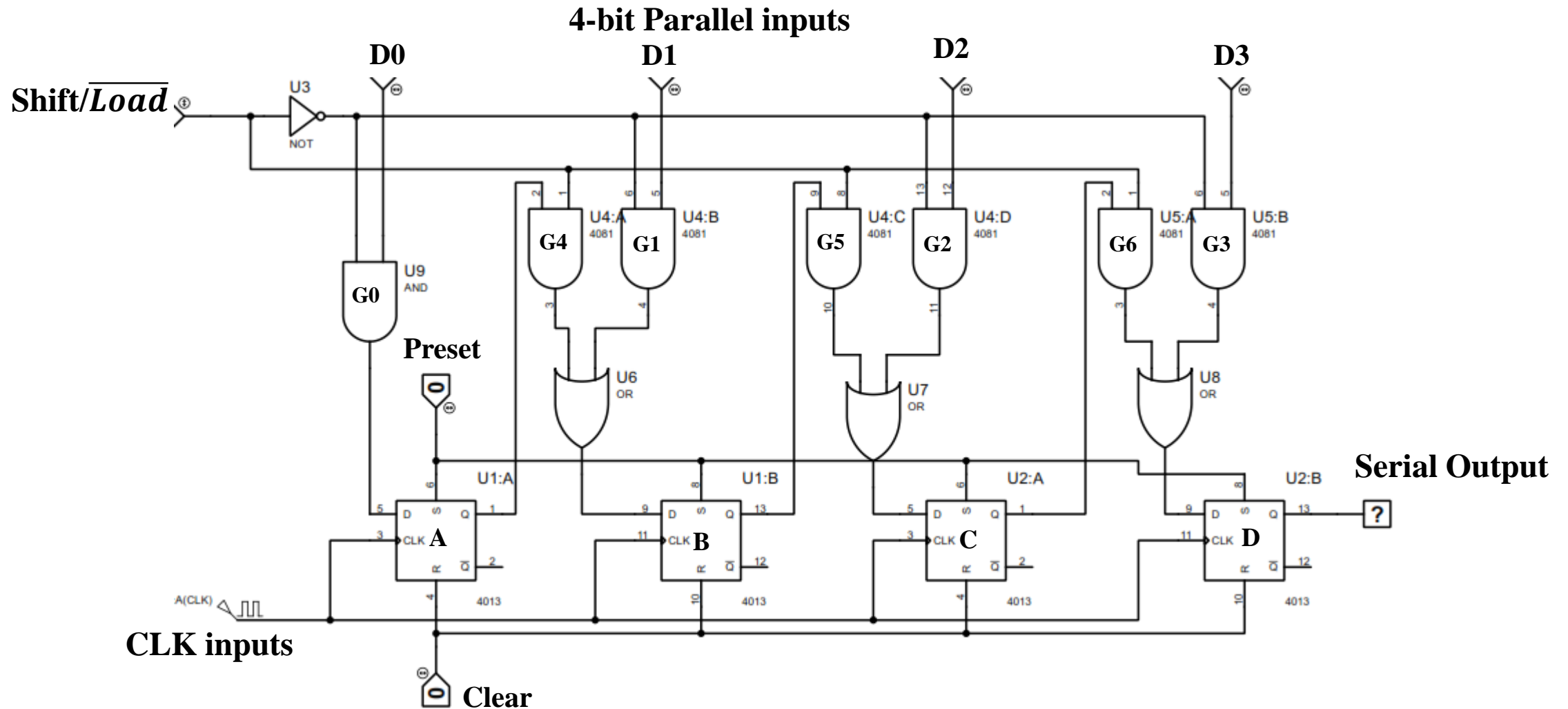iii. *Parallel-in to Serial-out (SISO) Shift Register*

- **4-bit Parallel-in to Serial-out Shift Register**





Operation:

- Data are entered parallel but taken in a serial mode.
- When **Shift/ \overline{Load} =LOW**; $G0, G1, G2, G3$ gates are enabled, allowing to pass data $D0, D1, D2, D3$ to flip-flop (A-D) input D parallelly.
- When **Shift/ \overline{Load} =HIGH**; $G4, G5, G6$ gates are enabled, allowing bits to shift right from one stage to another on each clock pulse.
- Output is taken at Q_D serially.

Let us consider an input data as, $D_0D_1D_2D_3=(1010)$.

On a 1st clock pulse, **Shift/Load=LOW**; so, parallel data (1010) get loaded into register, making $Q_D = 0$.

On 2nd clock pulse, **Shift/Load=HIGH**; data (1010) get shifted right into register, making $Q_D = 1$ and so on.

	Register Content				
CLK	Q_A	Q_B	Q_C	Q_D	Remarks
1	1	0	1	0	Data entered parallelly 
2	0	1	0	1	
3	0	0	1	0	
4	0	0	0	1	Data leaving serially 
5	0	0	0	0	


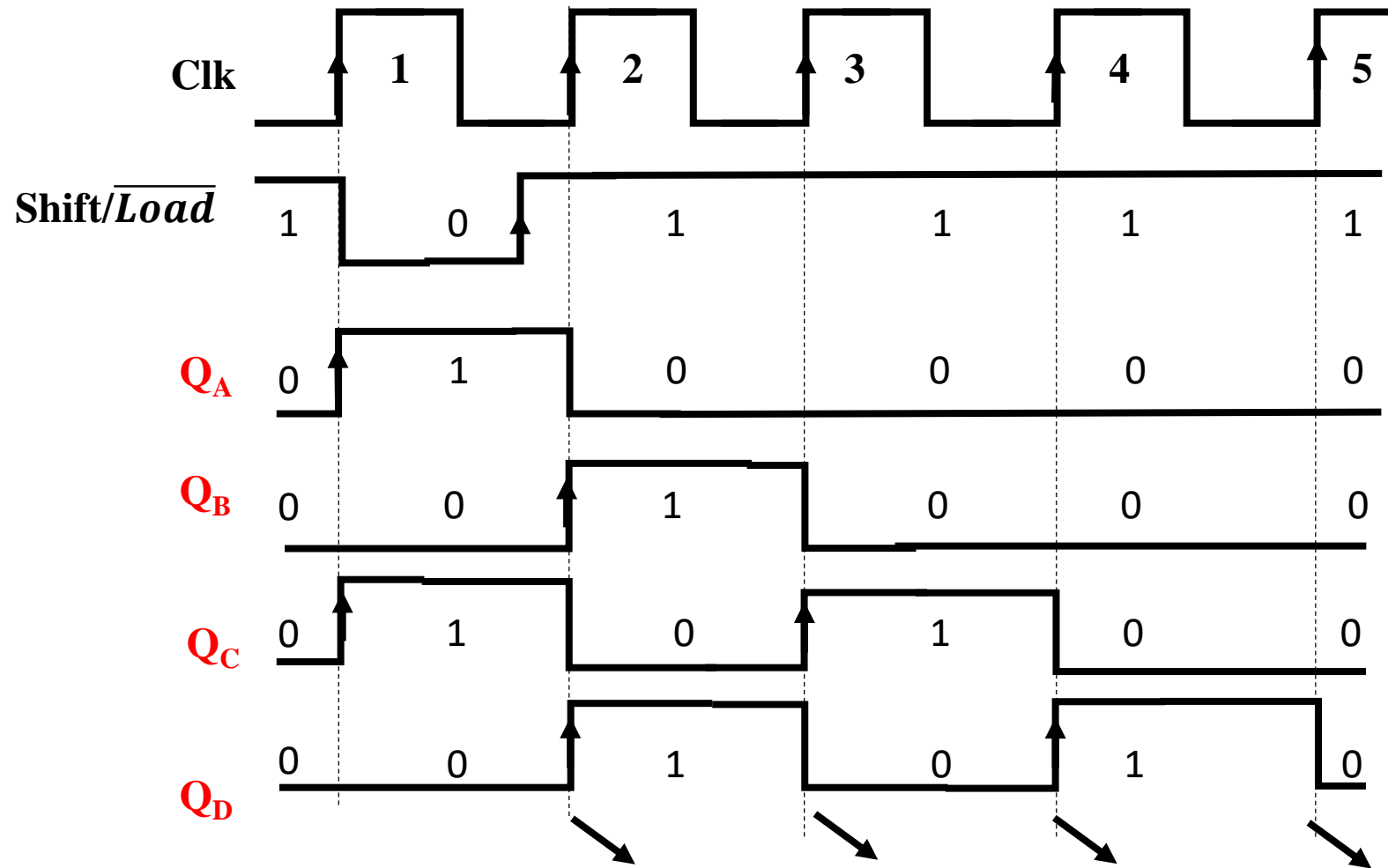


Fig: Timing Diagram for storing 1010 in PISO shift register

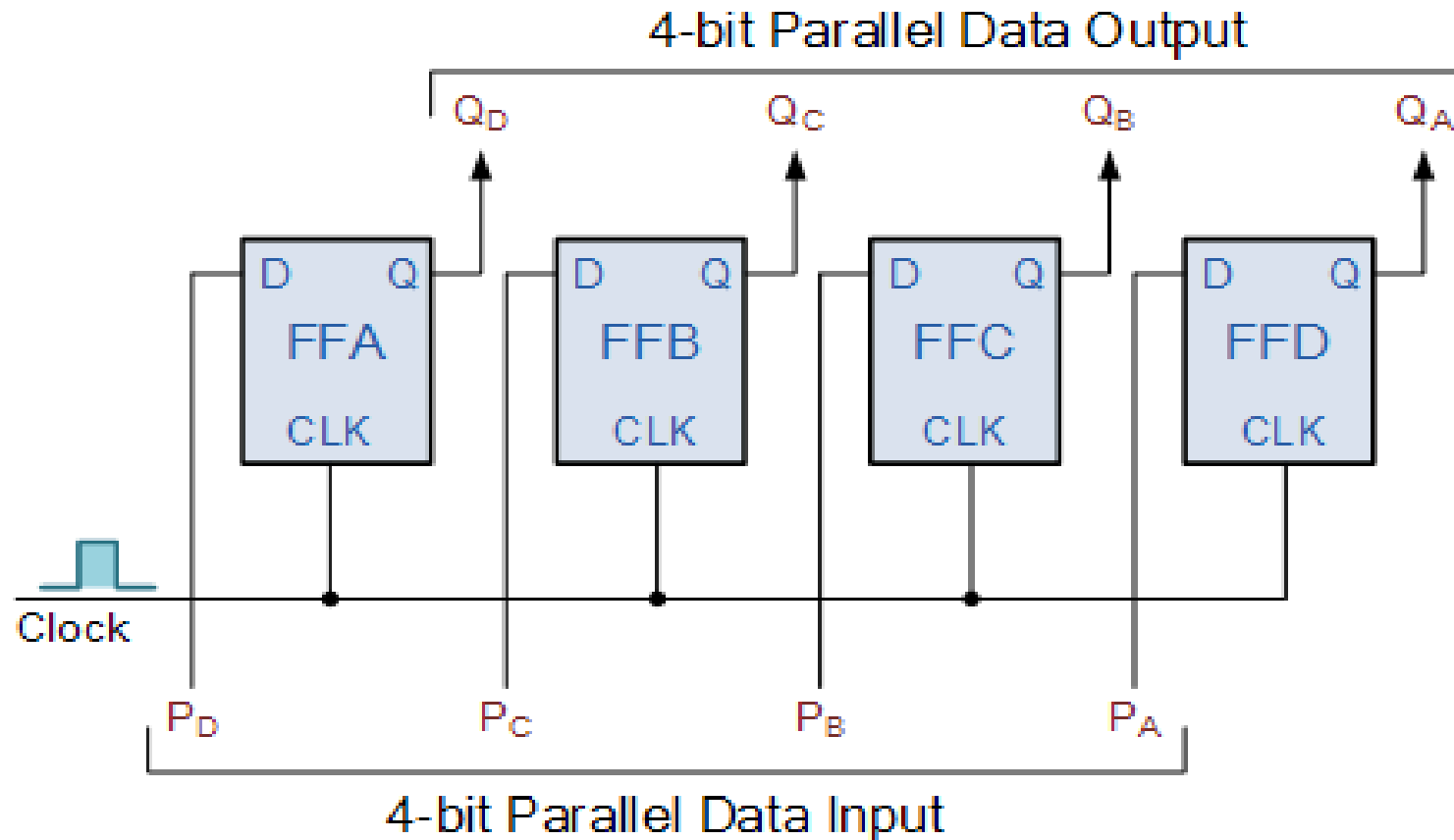
iv. Parallel-in to Parallel-out (SISO) Shift Register

- **4-bit Parallel-in to Parallel-out Shift Register**



Bi-directional Shift register

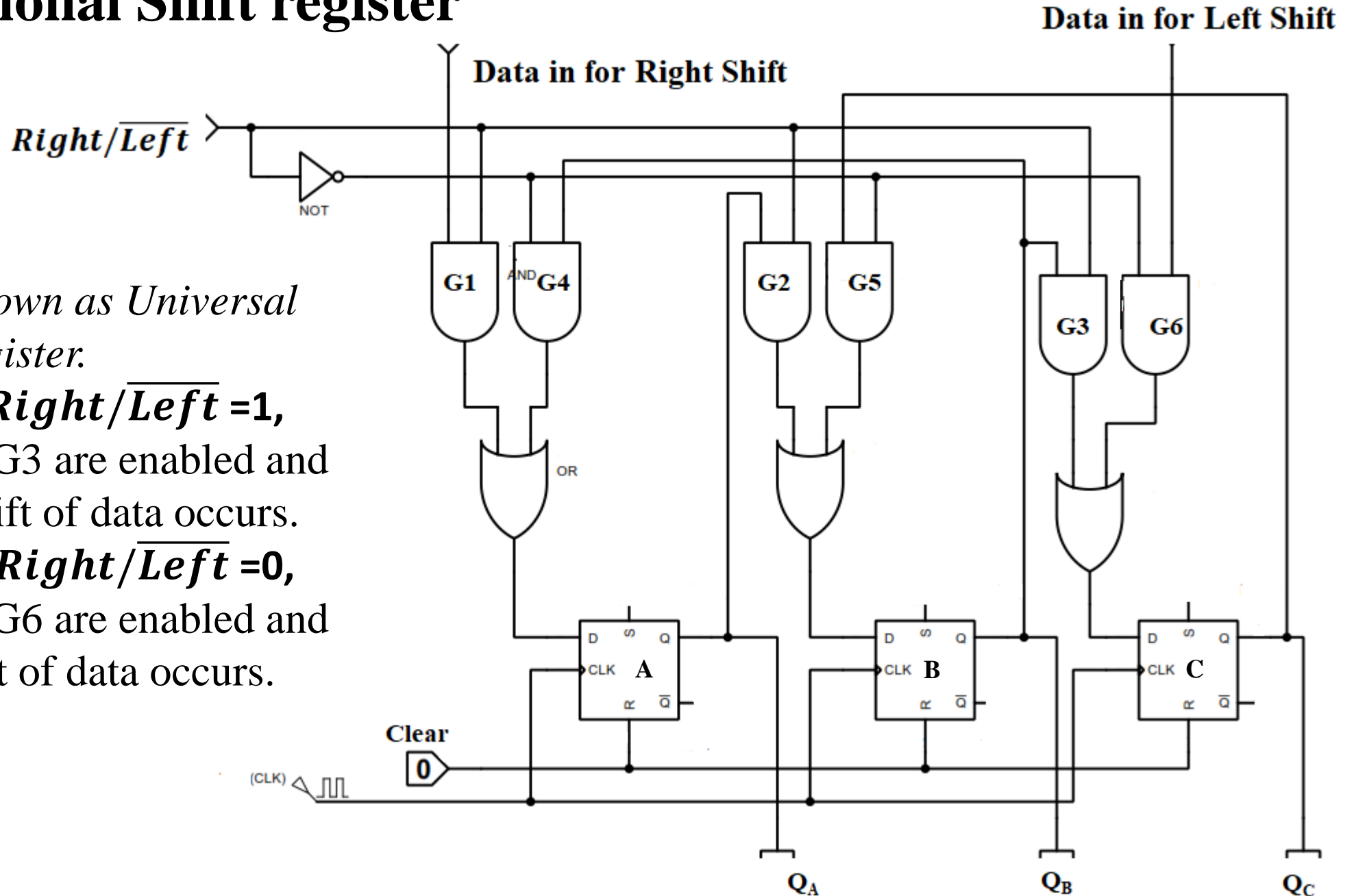- Also known as Universal shift register.
- i. When ***Right/Left*** = 1, G1, G2, G3 are enabled and right shift of data occurs.
- ii. When ***Right/Left*** = 0, G4, G5, G6 are enabled and left shift of data occurs.



Ring Counter

- Typical application of shift register.
- The only change in the output of last FF is connected to the input of first FF.
- ***No. of states = no. of FF used in this case*** (Special case).
- Used to control the sequence of stepper motor.
- E.g.: Initial register pattern values 1000

CLK	Q _A	Q _B	Q _C	Q _D
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	0	0	0

Note: In counter, no. of states are generally the max. limit up to which counter can count, given by 2^n , where n =no. of bits used.

Johnson Counter

- Also known as *Switch-Tail counter*.
- Eliminates the limitation of ring counter.
- The complement output of last FF is connected to the input of first FF.

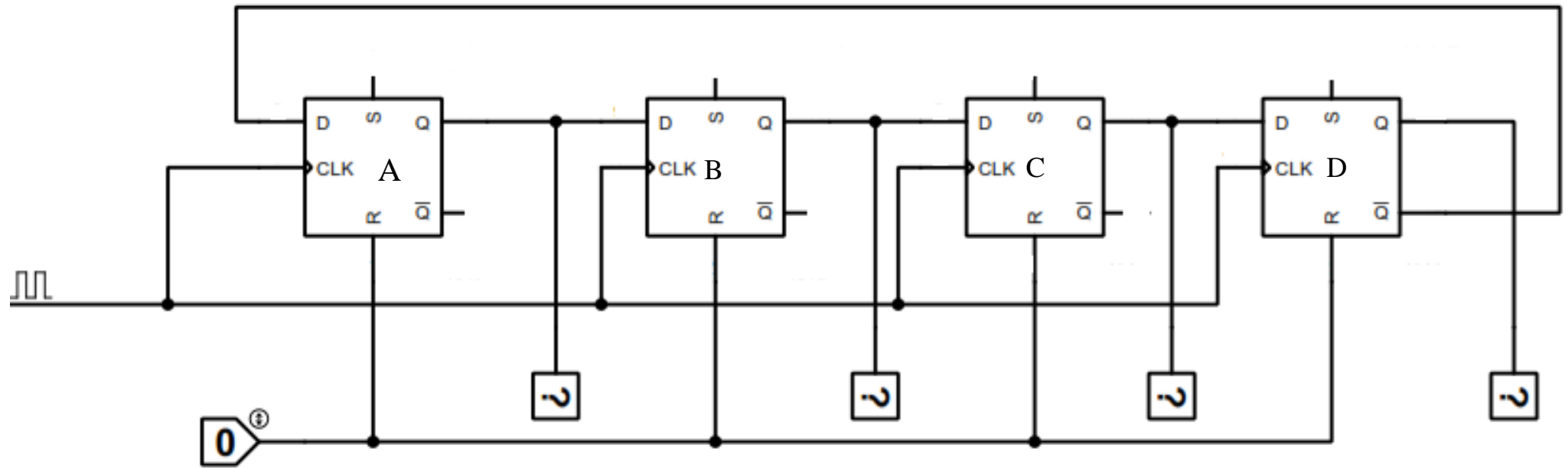


Fig: Logic Diagram of Johnson Counter

Initially, **Clear =1**, to reset the FFs to 0000 State.

CLK	Q_A	Q_B	Q_C	Q_D
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	0	0	1	1
6	0	0	0	1
7	0	0	0	0