

UNIT 4/5

COMBINATIONAL LOGIC

2ND SESSION

Implementation of Boolean functions using Decoder and Multiplexers

1. Using Decoder

- Any combinational circuit with 'n' inputs and 'm' outputs can be implemented with 'n to 2^n ' decoder with 'm' OR gate.
- Ex:** *Implement the following Boolean expression using decoder:*

$F1 = \sum m(0,4,6)$, $F2 = \sum m(0,5)$ and $F3 = \sum m(1,2,3,7)$ where F is the function of A,B,C.

No. of Inputs=3

Decoder size=3:2³=3:8


No of outputs=3 (F1,F2,F3)

No, of OR gate=3

$$F1 = \sum m(0,4,6) = m_0 + m_4 + m_6 = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}BC$$

$$F2 = \sum m(0,5) = m_0 + m_5 = \bar{A}\bar{B}\bar{C} + A\bar{B}C$$
 
$$F3 = \sum m(1,2,3,7) = m_1 + m_2 + m_3 + m_7 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC$$



Ex: *Implement of the Full Adder using decoder:*

No. of Inputs=3


Decoder size=3:2³=3:8

No of outputs=2 (Sum and Carry)

No, of OR gate=2

$$\text{Sum (S)} = \sum m(1,2,4,7) = m1 + m2 + m4 + m7 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$
 
$$\text{Carry (C)} = \sum m(3,5,6,7) = m3 + m5 + m6 + m7 = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$




2. Using Multiplexer

- The inputs of the Boolean function are the selection lines of the MUX.
- **Ex:** *Implement the function $F(A,B,C)=\sum m(1,2,6,7)$*



no. of variables = 3 = no. of selection lines

 size of MUX = $2^3 \times 1 = 8 \times 1$



Seven Segment Decoder

  - An electronic device which consists of seven light emitting diodes (LEDs) arranged in a some definite pattern (common cathode or common anode type),
- Display hexadecimal numerals(input is BCD i.e., 0-9).



	INPUT				OUTPUT						
Digits	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

Truth Table for common cathode

From the above truth table, the Boolean expressions of each output functions can be written as;

$$a = F1 (A, B, C, D) = \sum m (0, 2, 3, 5, 7, 8, 9)$$

$$b = F2 (A, B, C, D) = \sum m (0, 1, 2, 3, 4, 7, 8, 9)$$

$$c = F3 (A, B, C, D) = \sum m (0, 1, 3, 4, 5, 6, 7, 8, 9)$$


$$d = F4 (A, B, C, D) = \sum m (0, 2, 3, 5, 6, 8)$$

$$e = F5 (A, B, C, D) = \sum m (0, 2, 6, 8)$$

$$f = F6 (A, B, C, D) = \sum m (0, 4, 5, 6, 8, 9)$$

$$g = F7 (A, B, C, D) = \sum m (2, 3, 4, 5, 6, 8, 9)$$

K-Map Simplification

 

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	x	x	x	x
10	1	1	x	x

$$a = A + C + BD + \overline{B}\overline{D}$$

AB \ CD	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	x	x	x	x
10	1	1	x	x

$$b = \overline{B} + \overline{C}\overline{D} + CD$$

AB \ CD	00	01	11	10
00	1	1	1	0
01	1	1	1	1
11	x	x	x	x
10	1	1	x	x

$$c = B + \overline{C} + D$$

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	x	x	x	x
10	1	1	x	x

$$d = \overline{B}\overline{D} + C\overline{D} + B\overline{C}D + \overline{B}C + A$$

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	x	x	x	x
10	1	0	x	x


$$e = \overline{B}\overline{D} + C\overline{D}$$

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	x	x	x	x
10	1	1	x	x

$$f = A + \overline{C}\overline{D} + B\overline{C} + B\overline{D}$$

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	1	0	1
11	×	×	×	×
10	1	1	×	×
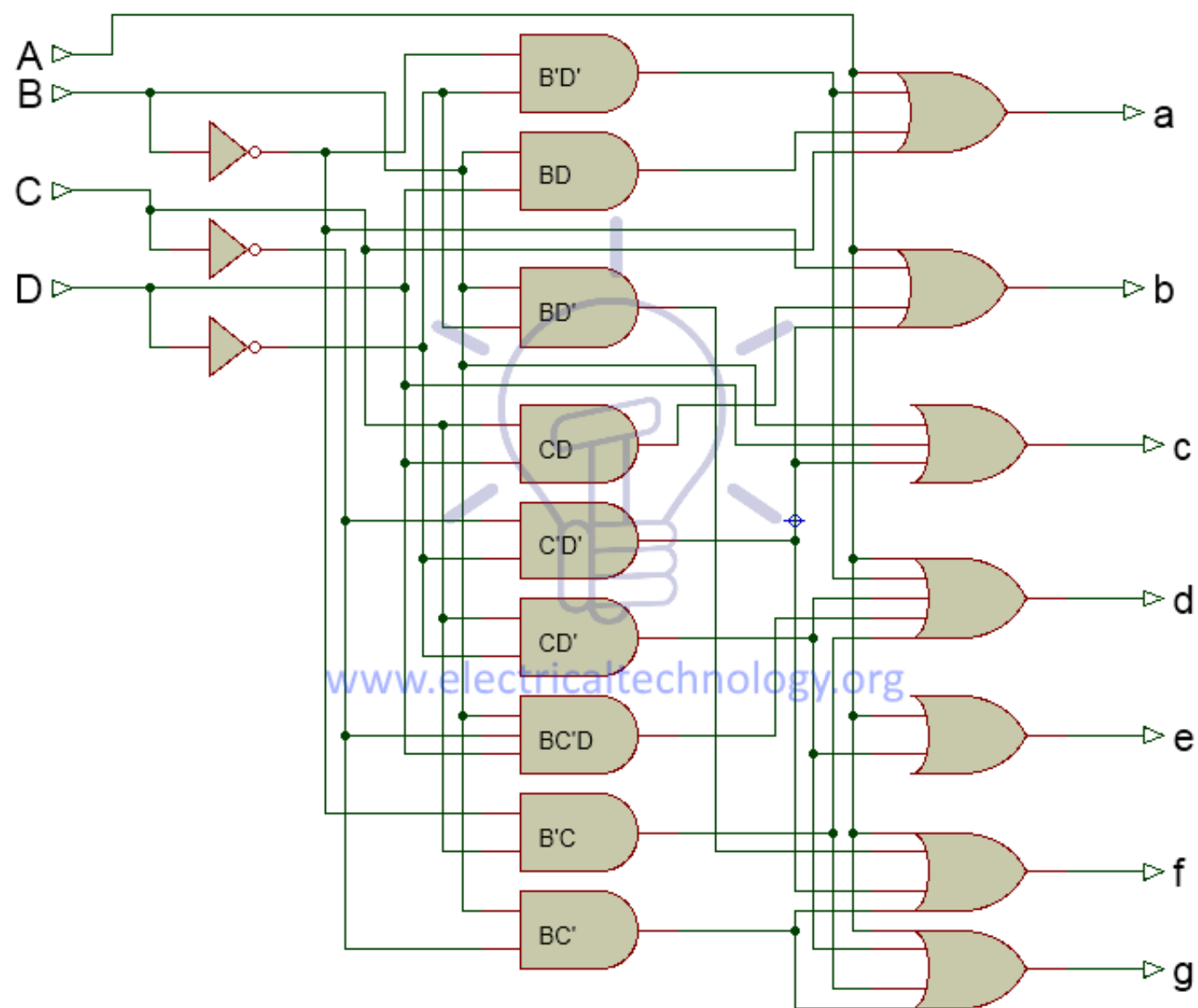
$$g = \overline{B}C + C\overline{D} + B\overline{C} + B\overline{C} + A$$



Schematic of BCD to 7-Segment Decoder

Magnitude Comparator


- A combinational circuit that **compares two digits or binary numbers** in order to find out whether one binary number is equal, less than or greater than the other.
- Three output terminals, one for $A > B$ condition, one for $A = B$ condition and one for $A < B$ condition.



Fig: Block diagram for n-bit comparator

1-Bit Magnitude Comparator

 - Compares two bits.
- Two inputs each for two single bit numbers and three outputs.



A	B	G (A>B)	L (A<B)	E (A=B)
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

Fig: Block diagram for 1-bit comparator

Truth Table

From the above truth table, the Boolean expressions of each output functions can be written as;

$$G = A\bar{B}$$

$$L = \bar{A}B$$

$$E = \bar{A}\bar{B} + AB = A \odot B$$

 


Fig: Circuit diagram for 1-bit comparator

2-bit comparator

A1	A0	B1	B0	A>B	A<B	A=B
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

Truth Table

For G (A>B)

		A>B			
		B1B0	00	01	11
A1A0	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

$$G (A>B) = A1B1' + A0B1'B0' + A1A0B0'$$

For G (A=B)

		A = B			
		B1B0	00	01	11
A1A0	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

$$E (A=B) = (A0 \odot B0) (A1 \odot B1)$$

For L (A<B)

$A < B$

B_1B_0	00	01	11	10
A_1A_0				
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

$$L(A < B) = A_1'B_1 + A_0'B_1B_0 + A_1'A_0'B_0$$

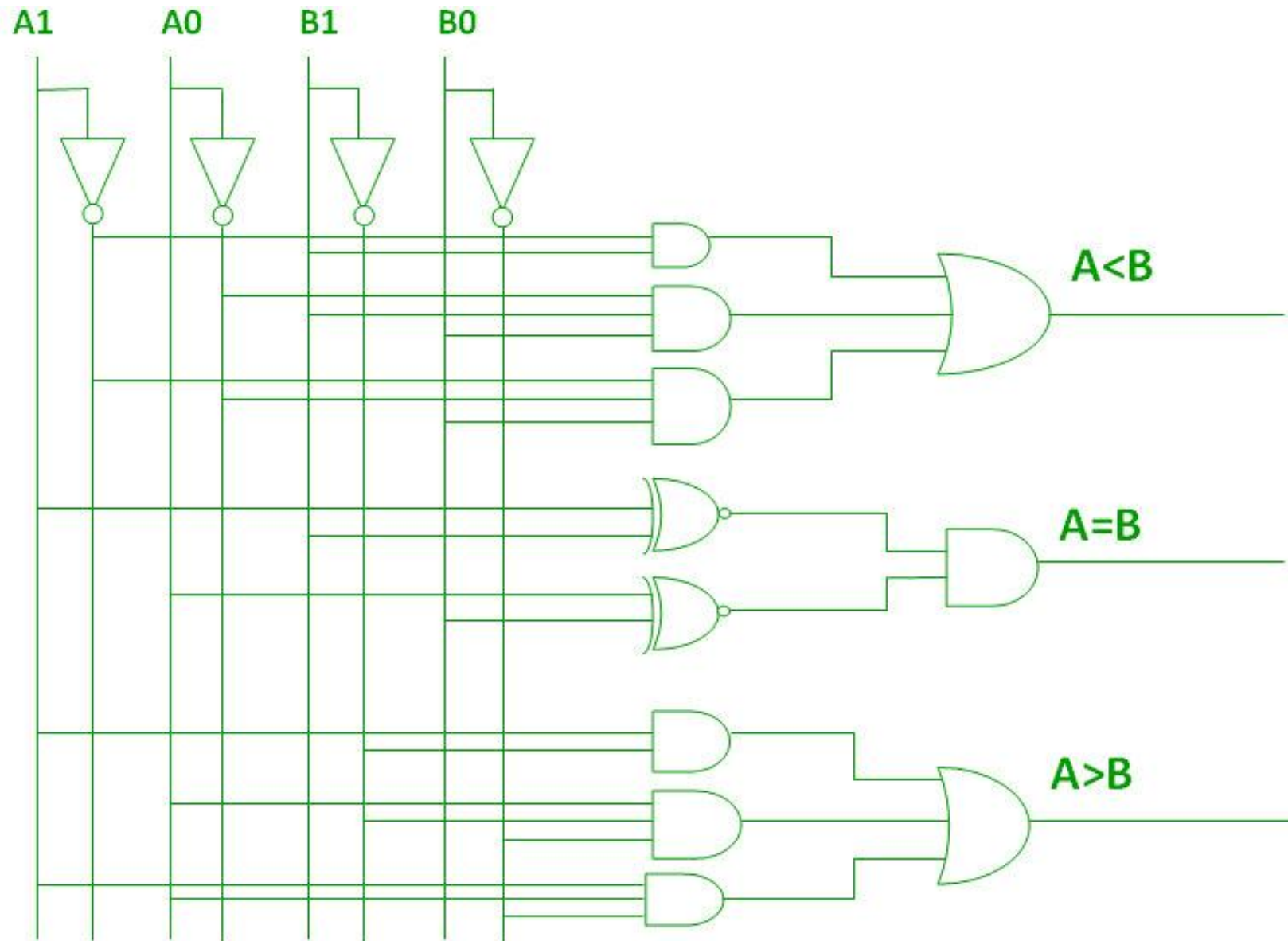


Fig: Circuit diagram for 2-bit comparator

Parity Generator and Checker

- 3-bit odd parity generator:

$$P = \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + AB\bar{C}$$
$$= A \odot (B \oplus C)$$

K-map

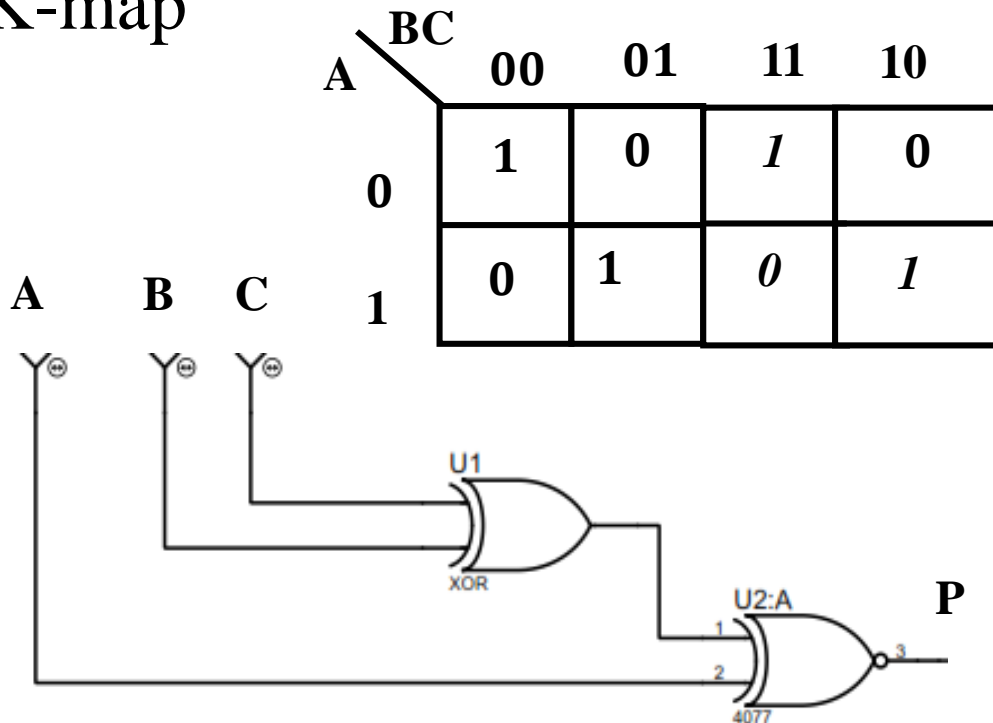


Fig: Circuit diagram for 3-bit odd parity generator

Information	Odd Parity bit
ABC	P
000	1
001	0
010	0
011	1
100	0
101	1
110	1
111	0

4-bit odd parity checker:

K-map

AB \ CP		CP			
		00	01	11	10
AB	00	1	0	1	0
	01	0	1	0	1
	11	1	0	1	0
	10	0	1	0	1

$$C_p = (A \odot B)(C \odot P) + (A \oplus B)(C \oplus P)$$

$$\text{Let } X = A \oplus B \text{ AND } Y = C \oplus P$$

$$\therefore C_p = X \odot Y$$

4-bit received message				Parity error check C_p
A	B	C	P	
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

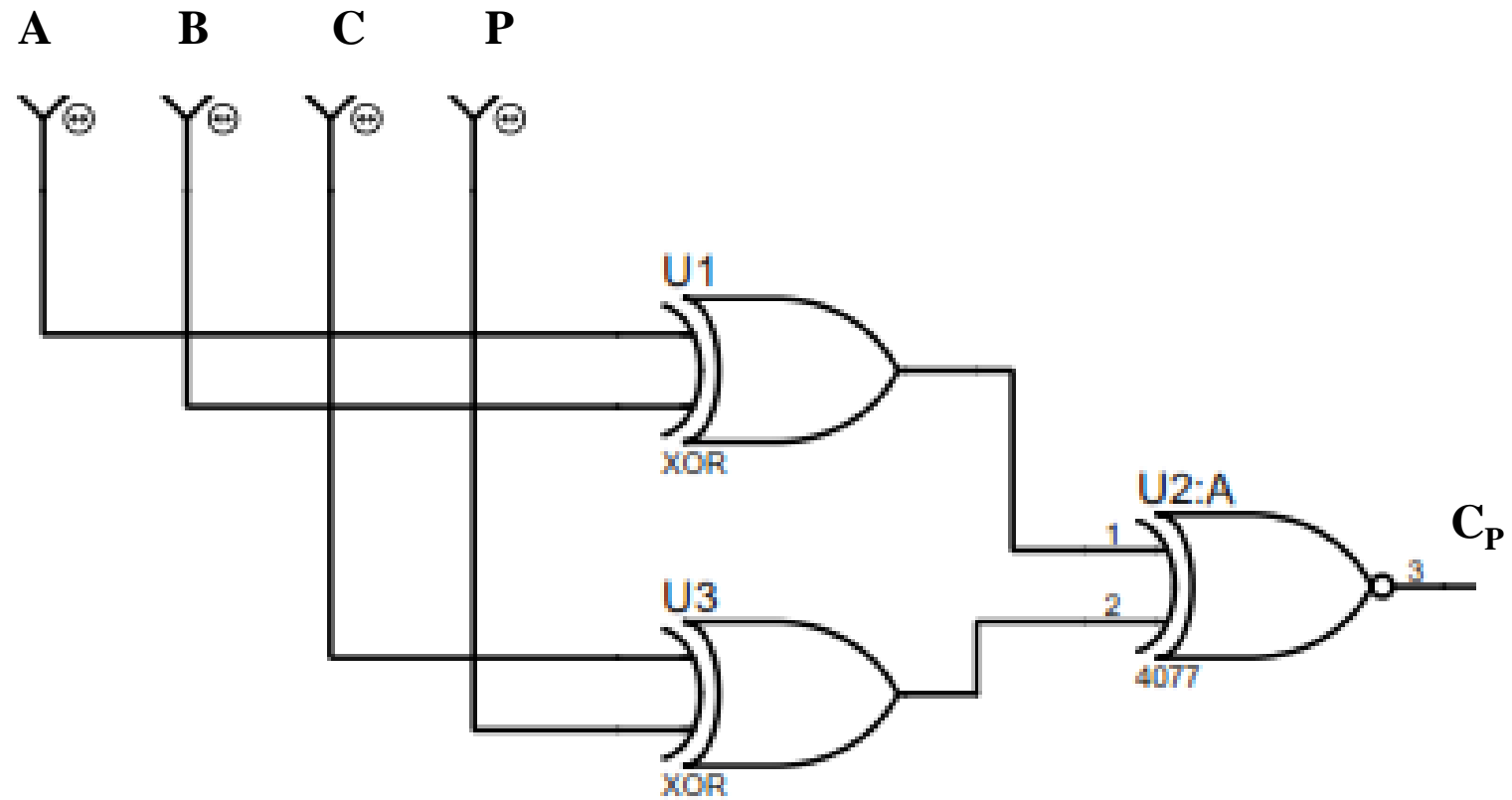


Fig: Circuit diagram for 4-bit odd parity checker

Read only Memory

- **Read Only Memory (ROM)**-Memory (Storage) device
- Special links that can be fused or broken to store data.
- Non-volatile


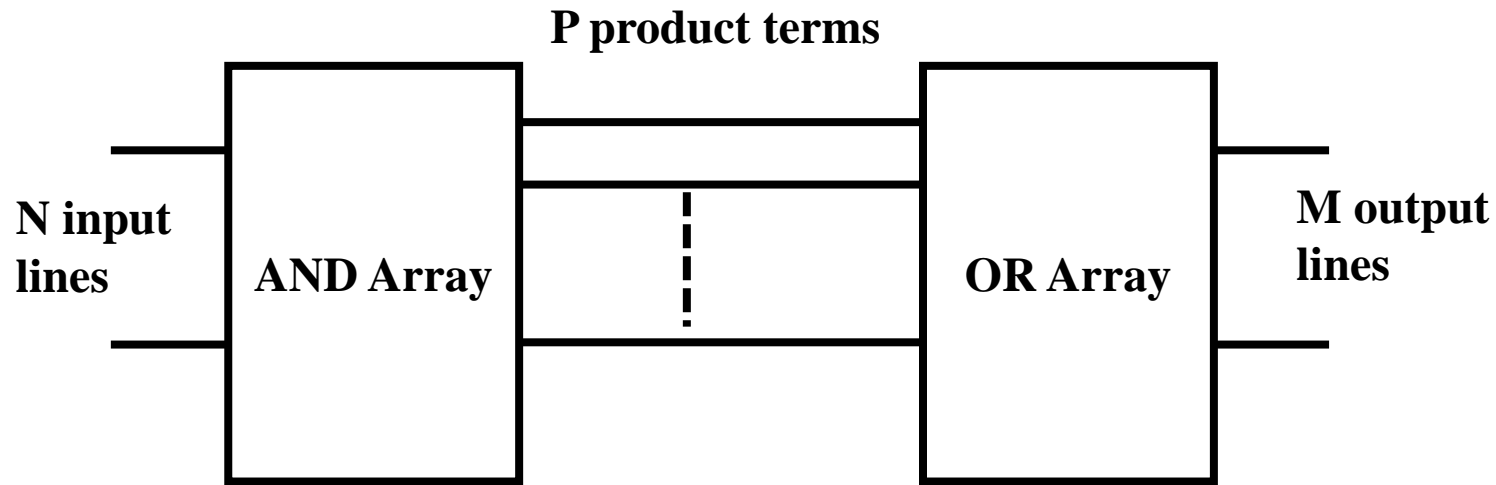


Fig: Block diagram of ROM

 

Internal construction of 64x4 ROM

Types:

1. Mask ROM (MROM)
2. Programmable ROM (PROM)
 - a. **Electrically Erasable and Programmable ROM (EEPROM)**
 - b. **Ultraviolet EPROM (UV EPROM)**
4. FLASH ROM

 


Fig: Block diagram of PROM

Programmable Array Logic (PAL)

- Most common one time programmable (OTP) logic device.
- Implemented with bipolar technology (TTL or ECL).

 


Fig: Block diagram of PAL

Programmable Logic Array (PLA)

- Also called Field Programmable Logic array (FPLA).
- User programs as per his/her requirement.

 


Fig: Block diagram of PLA

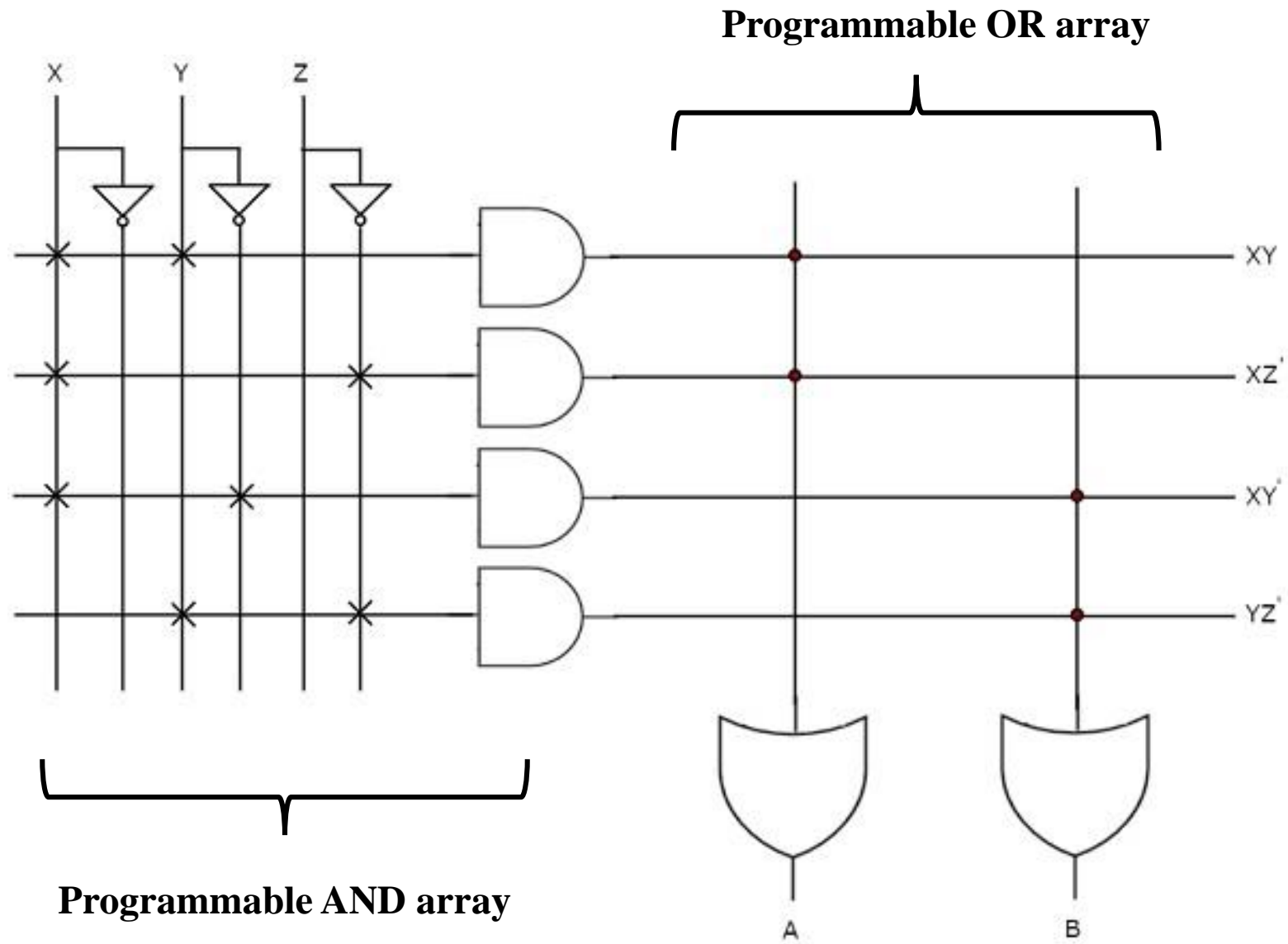


Fig: Circuit diagram of PLA

EX: Implement function using PLA:


$$F_0 = \sum m(0,1,4,6), F_1 = \sum m(2,3,4,6,7), F_2 = \sum m(0,1,2,6)$$

$$F_0 = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + AB\overline{C} = \overline{A}\overline{B} + A\overline{C}$$

$$F_1 = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C} + ABC = B + A\overline{C}$$

$$F_2 = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C} = \overline{A}\overline{B} + B\overline{C}$$

Product	Inputs			Outputs		
	<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> ₀	<i>F</i> ₁	<i>F</i> ₂
$\overline{A}\overline{B}$	0	0	-	1	0	1
$A\overline{C}$	1	-	0	1	1	0
<i>B</i>	-	1	-	0	1	0
$B\overline{C}$	-	1	0	0	0	1

 

References

- **M. Morris Mano**, “Digital Logic & Computer Design”
- **Brain Holdsworth**, “Digital Logic Design”, Elsevier Science.
- **John Patrick Hayes**, “Introduction to Digital Logic Design”, **Addison-Wesley**.
- **M. Morris Mano and Charles Kime**, “Logic and Computer Design Fundamentals”, Pearson New International.
- Wikipedia/Geeks For Geeks/Electronics Hub